
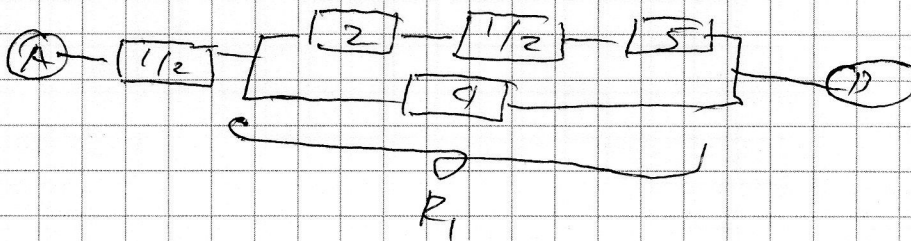
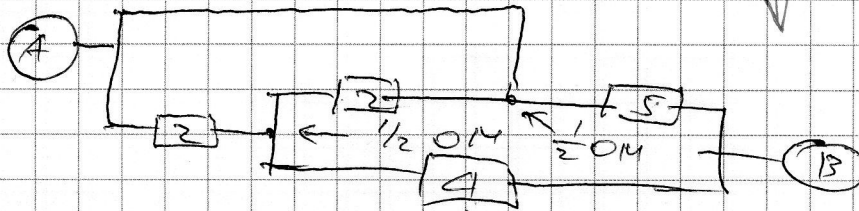


5

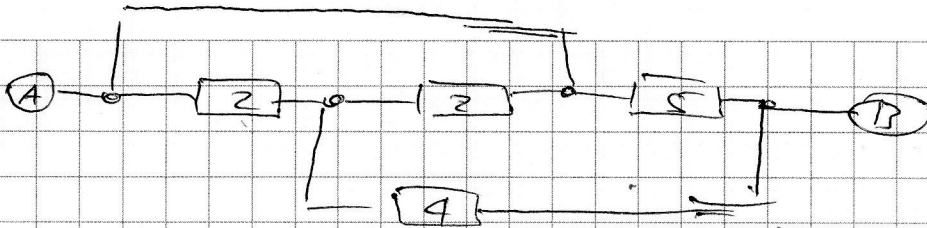

$$\frac{1}{R_1} = \frac{1}{4} + \frac{1}{7,5} = \frac{15}{60} + \frac{8}{60} = \frac{23}{60}$$

$$R_1 \approx 2,6 \text{ Ом}$$

$$R_{\text{общ.}} = 2,6 \text{ Ом} + 0,5 = 3,1 \text{ Ом}$$

Ответ: $R_{\text{общ.}} = 3,1 \text{ Ом}$